

## Experiment: 17


### PHASE SHIFT IN LCR CIRCUITS

**AIM:** To study the phase shift between voltage and current in a given series LCR circuit using a CRO and to draw a phasor diagram.

#### **APPARATUS:**

Capacitors ( $0.01\ \mu F$ ), Resistors ( $330\Omega$ ,  $1K\Omega$ ), Signal Generator, Bread board, CRO with probe

#### **CIRCUIT DIAGRAM:**

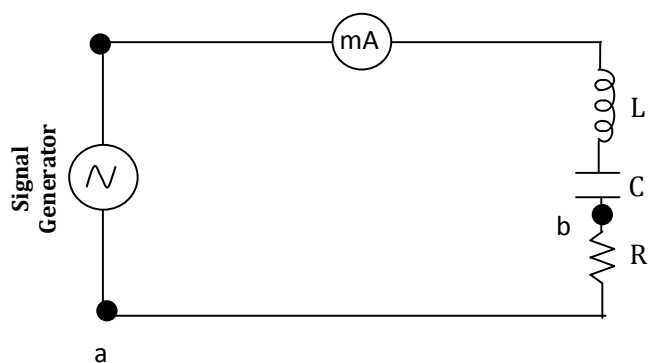


#### **FORMULA:**

The phase shift  $\Phi = \frac{\Delta T}{T} \times 360^\circ$  in degree

Where  $\Delta T$  is the time phase shift between the current (actually the voltage across the resistor) and the voltage across the function generator and  $T$  is the period of the sine wave generated ( $1/f$ ).

#### **WAVEFORM:**

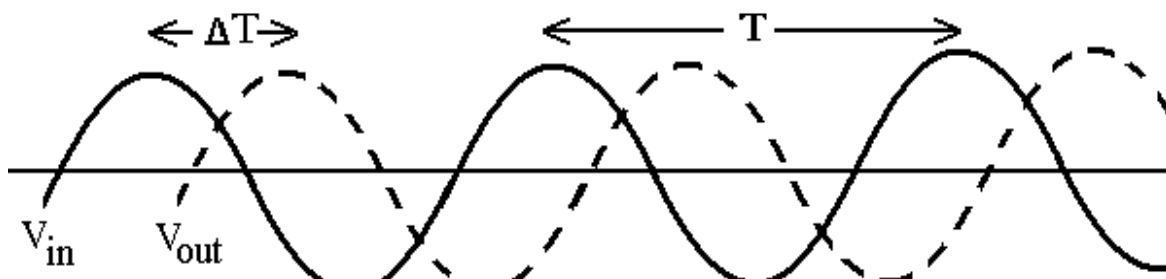

**TABULAR COLUMN:**

Frequency (Hz) <b>f</b>	$\Delta T$ (s) $\Delta t \times \text{Time Constant}$	$\Phi = \Delta T \times f \times 360^\circ$ (degree)
3000		
8000		

**PHASOR DIAGRAM for series LCR circuit:**

f=.....Hz

C= 0.01 $\mu$ FR=330 $\Omega$ 

L=0.1H

$V_L$ (V)	$V_C$ (V)	$V_R$ (V)	$X_L = 2 \pi f L$ ( $\Omega$ )	$X_C = 1/(2 \pi f C)$ ( $\Omega$ )	$\theta = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$ (deg)

**Procedure:**

1. Measure the voltages across inductor ( $V_L$ ), capacitor ( $V_C$ ) and resistor ( $V_R$ ) using AC voltmeter.
2. Since the current flowing through the circuit is common to all three circuit elements, mark this as the reference vector.
3. Draw the three voltage vectors relative to this at their corresponding phase angles.
4. The resulting vector  $V_S$  is obtained by adding together two of the vectors,  $V_L$  and  $V_C$  and adding this sum to the remaining vector  $V_R$ .

5. The angle made by the resultant vector  $V_S$  with  $V_R$  gives the phase difference between voltage and current in series LCR circuit. As shown in the Fig 2, the resultant voltage leads the current by an angle  $\theta$ .

6. If  $X_L > X_C$ ,  $\tan\theta$  is positive, and applied voltage leads the current by phase angle  $\theta$ .

If  $X_L < X_C$ ,  $\tan\theta$  is negative and applied voltage lags behind the current by phase angle  $\theta$ .

The phase angle  $\theta$  can also be calculated from R, L and C values, using  $X_L$  and  $X_C$  as:

$$\tan \theta = \frac{X_L - X_C}{R}$$

$$\theta = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

where, Inductive reactance  $X_L = 2\pi fL$  and Capacitive reactance  $X_C = \frac{1}{2\pi fC}$ .

**Result:** For a given series LCR circuit phase angle is measured using DSO,

i. For ..... Hz is ..... deg

ii. For..... Hz is ..... deg

And from phasor diagram for For..... Hz is ..... deg.